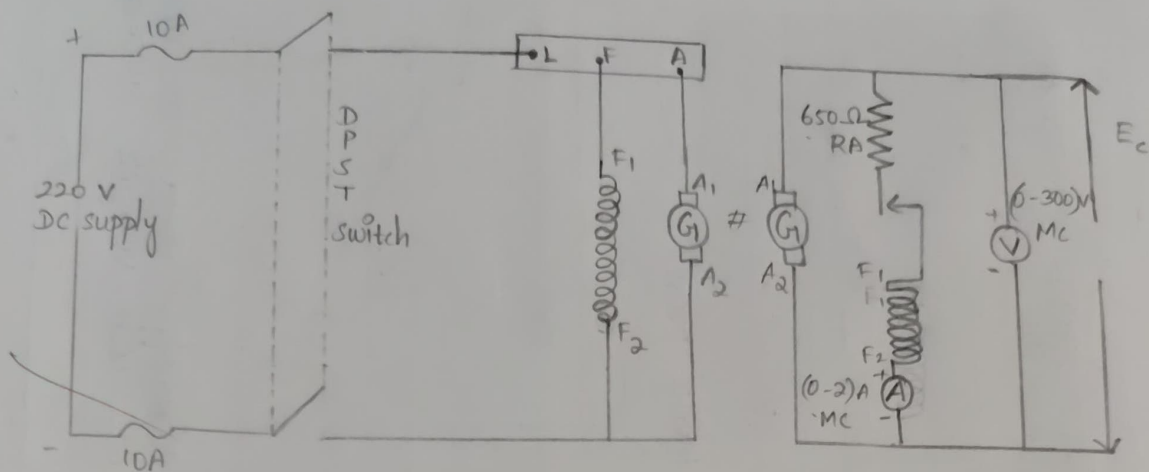


OPEN CIRCUIT CHARACTERISTICS



Expt. No. 02

DATE: 16/02/24

OPEN CIRCUIT AND LOAD CHARACTERISTIC OF DC SHUNT GENERATOR

AIM:

To draw the open circuit and load characteristics of DC shunt generator.

APPARATUS REQUIRED:

Laptop with Internet connection

THEORY:

DC generator converts mechanical energy into electrical energy.

DC generator works on the principle of Faraday's law. It states that "when a conductor cuts the magnetic flux and emf is induced".


The field winding and armature windings are connected in parallel in the shunt generator.

Open circuit characteristics

It is also known as magnetization characteristics or no load characteristics. It is a graph drawn

Page No. 4

LOAD CIRCUIT CHARACTERISTICS

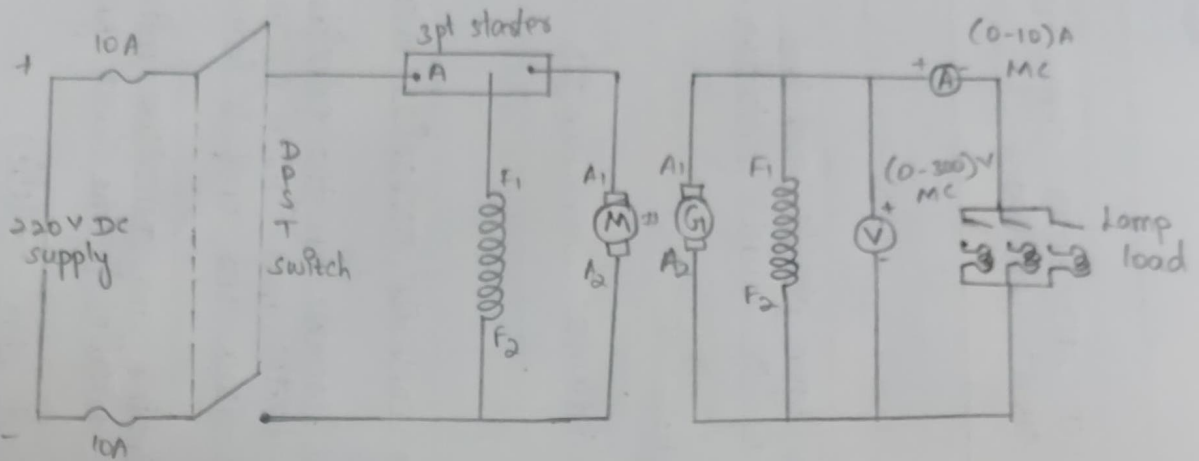

Expt. No.

Page No. 5

between open circuit voltage (E_o) and field current (I_f).

Load circuit characteristic

It is a graph drawn between load voltage (V_L) and load current (I_L). It is also known as external characteristics.


PROCEDURE :

Open circuit characteristic

1. Connections are made as per the circuit diagram.
2. Switch on the supply and note down the readings (voltage and current)
3. By varying the field rheostat different values of open circuit voltage and field current are noted.
4. Plot the graph between open circuit voltage and field current.

OPEN CIRCUIT CHARACTERISTICS

MODEL GRAPH:

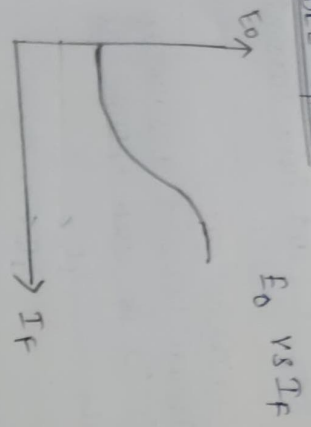

S.No	Voltage (V)	Current (A)
1.	115	0.16
2.	120	0.18
3.	126	0.20
4.	129	0.21
5.	133	0.23
6.	135	0.24
7.	138	0.28
8.	142	0.30

Expt. No.


Page No. 6

Load circuit characteristic:

1. Connections are made as per the circuit diagram.
2. Switch on the supply and note the no load voltage and current.
3. By connecting different loads, different values of load voltage and current.
4. Plot the graph between load voltage and load current.

LOAD CHARACTERISTICS

MODEL GRAPH:

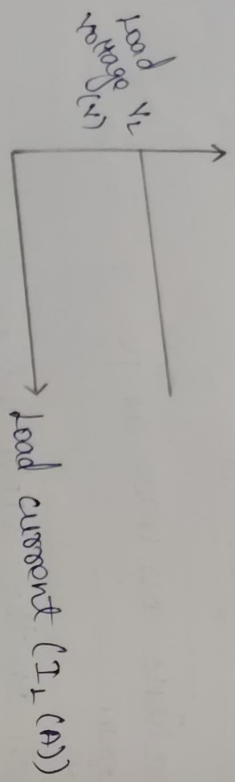


S.No	Current (A)	Voltage (V)
1.	1.2	2.20
2.	2.8	2.12
3.	3.2	2.08
4.	3.6	2.05
5.	5.5	2.00
6.	7	1.95

Expt. No.

Page No. 7


100



20/03/20

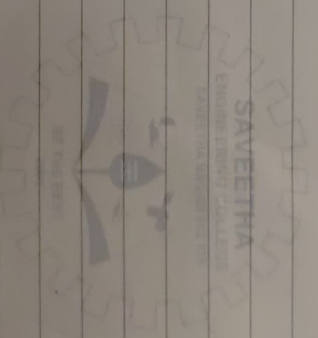

RESULT:

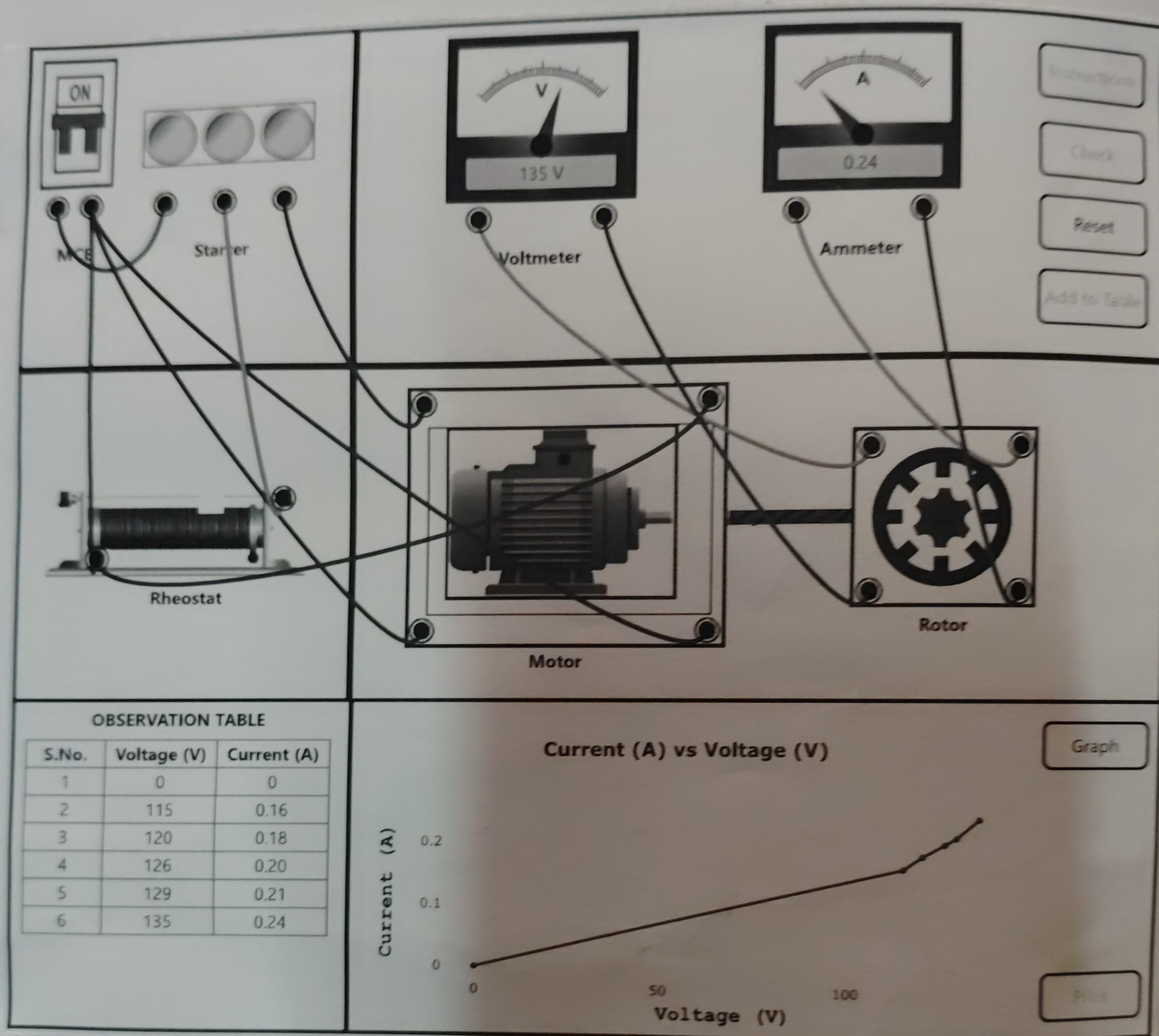Thus, the open circuit and load characteristics of DC shunt generator were verified successfully.



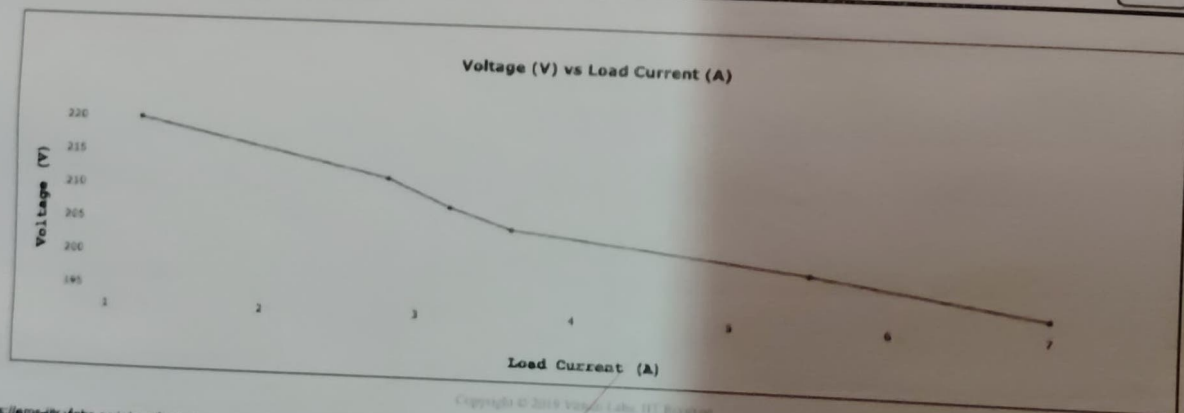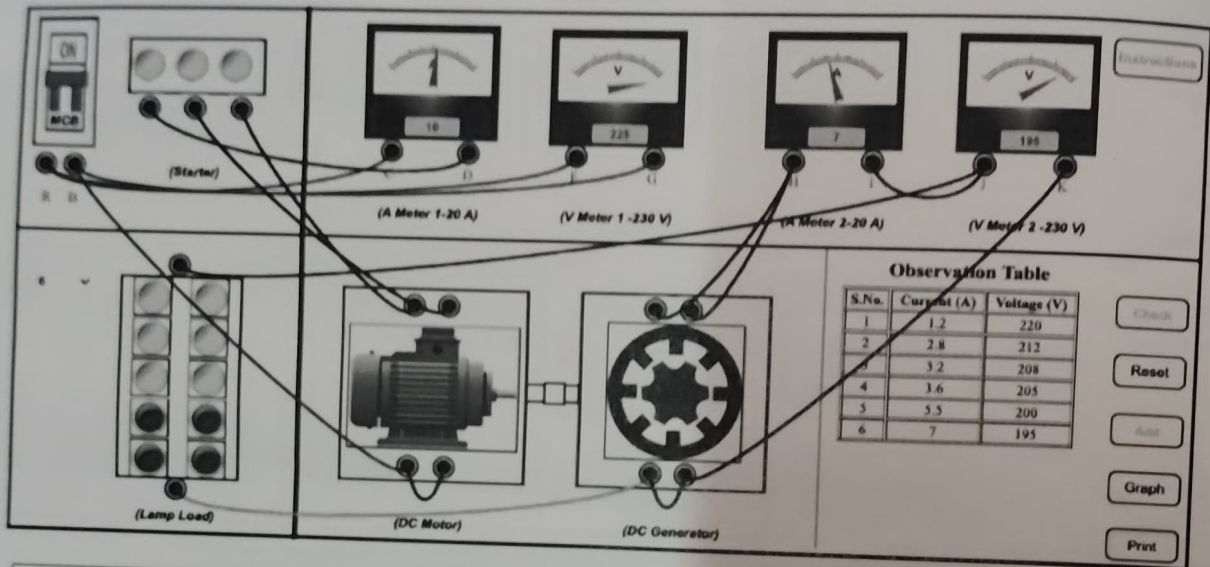

OPEN CIRCUIT CHARACTERISTIC


Scale:

x axis = 1cm = 0.02 A

y axis = 1cm = 10 V

$E_o (V)$

$I_f (A)$

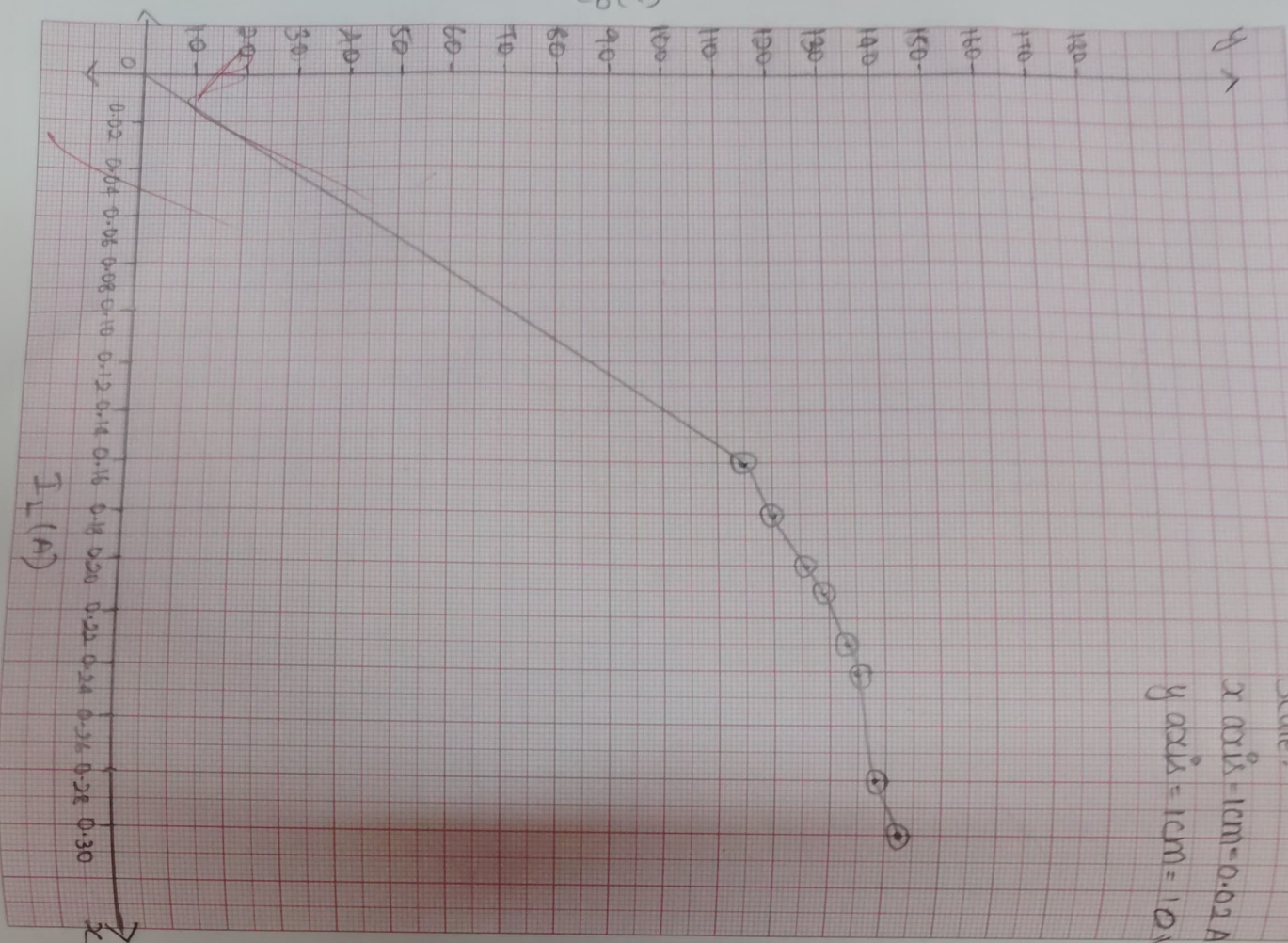

Expt. No. 02


OPEN CIRCUIT AND LOAD CHARACTERISTICS OF DC SHUNT GENERATOR

Page No.

Scale:

x axis = 1 cm = 1 A

y axis = 1 cm = 10 V

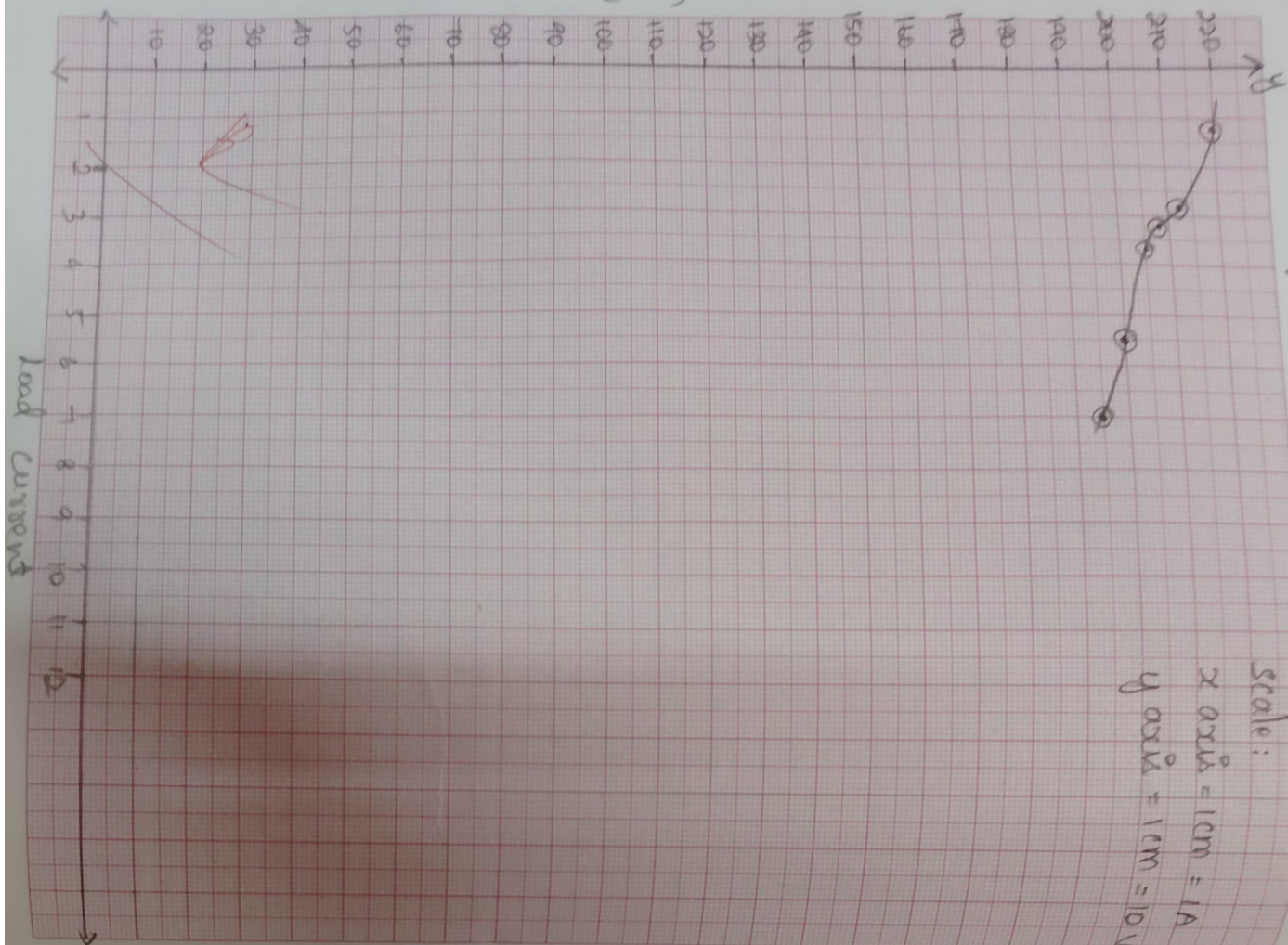

Expt. No. 02

OPEN CIRCUIT AND LOAD CHARACTERISTICS
OF DC SHUNT GENERATOR.

Page No.